ASSIGNMENT - 01

Team Member 2	M.SRIJA
Register Number	820319106019
Date	03 October 2022
Team ID	PNT2022TMID46406
Project Name	SIGNS WITH SMART CONNECTIVITY FOR BETTER
	ROAD SAFETY
Maximum Marks	2 Marks

Make a Smart Home in Tinkercad, using 2+ sensors, LED, Buzzer in single code and circuit.

Source code:

```
int t=2;
int e=3;
void setup() {
    Serial.begin(9600);
    pinMode(t,OUTPUT);
    pinMode(e,INPUT);
    pinMode(12,OUTPUT);
} void loop() {
    digitalWrite(t,LOW);
    digitalWrite(t,HIGH);
    delayMicroseconds(10);
    digitalWrite(t,LOW);
```

```
float dis=(dur*0.0343)/2;
Serial.print("Distance is: ");
Serial.println(dis);
if(dis>=100) {
digitalWrite(8,HIGH);
digitalWrite(7,HIGH);
}
if(dis>=100)
{
for(int i=0; i<=30000; i=i+10)
{
tone(12,i);
delay(1000);
noTone(12);
delay(1000);
}
}
double a= analogRead(A0);
double t=(((a/1024)*5)-0.5)*100;
Serial.print("Temp Value: "); S
Serial.println(t);
delay(1000);
if(t>=100) {
```

```
digitalWrite(8,HIGH);
digitalWrite(7,HIGH);
}
if(t>=100)
{
for(int i=0; i<=30000; i=i+10)
{
tone(12,i);
delay(1000);
noTone(12);
delay(1000);
}
}
if(t<100)
{
digitalWrite(8,LOW);
digitalWrite(7,LOW);
}
}
```

Circuit Diagram:

